



## Σχεδίαση Ψηφιακών Συστημάτων

ΕΞΑΜΗΝΙΑΙΑ ΑΣΚΗΣΗ ΘΕΩΡΙΑΣ

ΜΕΡΟΣ 04

Τμήμα Μηχανικών Πληροφορικής  
& Υπολογιστών

(Καθηγητής: Ιωάννης Βογιατζής)

Μάρκος Παντελιδάκης - 18390228 - [ice18390228@uniwa.gr](mailto:ice18390228@uniwa.gr)

# 1. Μνήμη Εντολών

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.std_logic_unsigned.all;
4  use ieee.numeric_std.all;
5
6  entity instruction_memory is port (
7      Addr : in std_logic_vector(3 downto 0);
8      C : out std_logic_vector(31 downto 0));
9  end instruction_memory;
10
11  architecture arch1 of instruction_memory is
12  type instr_array is array (0 to 15) of std_logic_vector (31 downto 0);
13  constant instr_mem: instr_array := (
14      "000000001000010000100000000100100", --0 and $4 $4 $4
15      "00000000110000100010100000100010", --1 sub $5 $2 $6
16      "1111111111111111111111111111111", --2
17      "0000000000000000000000000000000", --3
18      "1111111111111111111111111111111", --4
19      "0000000000000000000000000000000", --5
20      "00000000101001100010000000100000", --6 add $4, $5, $6
21      "1111111111111111111111111111111", --7
22      "1111111111111111111111111111111", --8
23      "1111111111111111111111111111111", --9
24      "1111111111111111111111111111111", --10
25      "1111111111111111111111111111111", --11
26      "1111111111111111111111111111111", --12
27      "1111111111111111111111111111111", --13
28      "1111111111111111111111111111111", --14
29      "1111111111111111111111111111111" --15
30  );
31  begin
32      C <= instr_mem(to_integer(unsigned(Addr)));
33  end arch1;

```


Εικ4.1.1: Κώδικας αρχείου VHDL κυκλώματος Μνήμης Εντολών MIPS.

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.std_logic_unsigned.all;
4  use ieee.numeric_std.all;
5
6  entity Instruction_memory_tb is
7  end Instruction_memory_tb;
8
9  architecture test_b of Instruction_memory_tb is
10     signal Addr1 : std_logic_vector(3 downto 0);
11     signal C1 : std_logic_vector(31 downto 0);
12
13     component Instruction_memory PORT(
14         Addr : in std_logic_vector(3 downto 0);
15         C : out std_logic_vector(31 downto 0));
16     end component;
17
18     BEGIN
19     M1 : Instruction_memory port map (Addr => Addr1, C => C1);
20
21     process
22     begin
23         Addr1 <= "0000"; wait for 50 ps;
24         Addr1 <= "0001"; wait for 50 ps;
25         Addr1 <= "0110"; wait for 50 ps;
26     end process;
27 end test_b;

```

Εικ4.1.2: Κώδικας αρχείου VHDL testbench κυκλώματος Μνήμης Εντολών MIPS.

 

Εικ4.1.3: Παράδειγμα κυματομορφής κυκλώματος Μνήμης Εντολών MIPS.

## 2. Μνήμη δεδομένων

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  USE ieee.std_logic_unsigned.all;
4  USE ieee.numeric_std.ALL;
5
6  entity dataMemory is port (
7      Addr   : in  std_logic_vector(5 downto 0);
8      writeD : in  std_logic_vector(31 downto 0);
9      we      : in  std_logic;
10     re      : in  std_logic;
11     clk     : in  std_logic;
12     readD   : out std_logic_vector(31 downto 0));
13  end dataMemory;
14
15  architecture behavioral of datamemory is
16
17      type memArray is array(0 to 63) of std_logic_vector(31 downto 0);
18      signal memfile : memArray;
19  begin
20      process(clk)
21      begin
22          if (clk'event and clk='0') then
23              if we='1' then
24                  memfile(to_integer(unsigned(Addr))) <= writeD;
25              end if;
26          end if;
27          if re='1' then
28              readD <= memfile(to_integer(unsigned(Addr)));
29          end if;
30      end process;
31  end behavioral;

```

Εικ4.2.1: Κώδικας αρχείου VHDL κυκλώματος Μνήμης δεδομένων MIPS.

```


1  library ieee;
2  use ieee.std_logic_1164.all;
3  USE ieee.std_logic_unsigned.all;
4  USE ieee.numeric_std.ALL;
5
6  entity dataMemory_tb is
7  end dataMemory_tb;
8
9  architecture test_b of dataMemory_tb is
10 signal Addr1 : std_logic_vector(5 downto 0);
11 signal writeD1 : std_logic_vector(31 downto 0);
12 signal we1 : std_logic;
13 signal re1 : std_logic;
14 signal clk1 : std_logic;
15 signal readD1 : std_logic_vector(31 downto 0);
16
17 component dataMemory PORT(
18     Addr    : in  std_logic_vector(5 downto 0);
19     writeD  : in  std_logic_vector(31 downto 0);
20     we      : in  std_logic;
21     re      : in  std_logic;
22     clk     : in  std_logic;
23     readD   : out std_logic_vector(31 downto 0));
24 end component;
25
26 BEGIN
27 M1 : dataMemory port map (Addr => Addr1, writeD => writeD1, we => we1, re => re1, clk => clk1, readD => readD1);
28 process
29 begin
30     clk1 <= '1'; wait for 50 ps;
31     we1 <= '1';
32     re1 <= '0';
33     Addr1 <= "000000";
34     writeD1 <= "010101010101010101010101010101";
35     clk1 <= '0'; wait for 50 ps;
36
37     clk1 <= '1'; wait for 50 ps;
38     Addr1 <= "000001";
39     writeD1 <= "11011101110111011101110111011101";
40     clk1 <= '0'; wait for 50 ps;
41
42     clk1 <= '1'; wait for 50 ps;
43     Addr1 <= "000010";
44     writeD1 <= "00100010001000100010001000100010";
45     clk1 <= '0'; wait for 50 ps;
46
47     clk1 <= '1'; wait for 50 ps;
48     Addr1 <= "000011";
49     writeD1 <= "10011001100110011001100110011001";
50     clk1 <= '0'; wait for 50 ps;
51
52     clk1 <= '1'; wait for 50 ps;
53     we1 <= '0';
54     re1 <= '1';
55     Addr1 <= "000000";
56     clk1 <= '0'; wait for 50 ps;
57
58     clk1 <= '1'; wait for 50 ps;
59     Addr1 <= "000001";
60     clk1 <= '0'; wait for 50 ps;
61 end process;
62 end test_b;

```

**Εικ4.2.2:** Κώδικας αρχείου VHDL testbench κυκλώματος Μνήμης δεδομένων MIPS.



**Εικ4.2.3:** Αναπαράσταση εγγραφής δεδομένων σε κυματομορφή στη μνήμη δεδομένων MIPS.

 

**Εικ4.2.4:** Αναπαράσταση ανάγνωσης δεδομένων σε κυματομορφή από τη μνήμη δεδομένων MIPS.